



**METRO STATE
UNIVERSITY**

**ICS 232 Computer Organization & Architecture
Homework 3 - Chapter 3 - 10 points
Due Date: 6/7/2023**

Name:

Note: Please post your homework to ICS232 D2L on or before the due date.

Chapter 3 – Boolean Algebra and Digital Logic

Essential Terms and Concepts

2. Which Boolean operation is referred to as a Boolean product?

AND

3. Which Boolean operation is referred to as a Boolean sum?

OR

12. Describe the operation of a ripple-carry adder. Why are ripple-carry adders not used in most computers today?

- ripple carry adder : output is known after the carry generated by the previous stage is produced
- too slow

18. How are sequential circuits different from combinational circuits?

- sequential : output is dependent on the current and previous input
- combinational : output is independent of time and relies on input at the particular instance

20. What do we mean when we say that a sequential circuit is edge triggered rather than level triggered?

- because the circuit is active at the positive/negative edge of the clock signal

24. Which flip-flop give a true representation of computer memory?

Data flip-flop / D flip-flop



METRO STATE UNIVERSITY

ICS 232 Computer Organization & Architecture Homework 3 - Chapter 3 - 10 points Due Date: 6/7/2023

Exercises

2. Construct a truth table for the following:

- a) $xyz + x(yz)' + x'(y+z) + (xyz)'$
b) $(x + y')(x' + z')(y' + z')$

4. Using DeMorgan's Law, write an expression for the complement of F if

$$F(x, y, z) = (x' + y)(x + z)(y' + z)'$$

$$y' + z + x'$$

10. Show that $x = xy + xy'$

- a) Using truth tables
b) Using Boolean identities

A) $2^2 = 4$

| X | Y | Y' | XY | XY' | XY + XY' |
|---|---|----|----|-----|----------|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 |

output
the operation's results
with addition for
each other

B) R.H.S. = $xy + xy'$
 $= x(y + y')$ [complementarity law]
 $= x(1) = (x \cdot 1)$ [property of 1 & 0]
 $= x = L.H.S$
 L.H.S = R.H.S

17. Simplify the following functional expressions using Boolean algebra and its identities.

List the identity used at each step.

A) $(xy + xz)(x' + z')$
 $(xx'y + xx'z + xyz' + xzz')$
 xyz'

- a) $x(y + z)(x' + z')$
 b) $xy + xyz + xy'z + x'y'z$ B) $xy + y'z$
 c) $xy'z + x(y + z')' + xy'z'$ xy'

23. The truth table for a Boolean expression is shown below. Write the Boolean expression in sum-of-products form.

$$\begin{array}{c} \text{num} \\ \downarrow \\ 2^3 = 8 \end{array}$$

$$\begin{array}{c} \text{num} \\ \downarrow \\ 2^3 = 8 \end{array}$$

| every 4th | every 2nd | every other |
|-----------|-----------|-------------|
| | | |

$$2^3 = 8$$

[illegible]



METRO STATE
UNIVERSITY

ICS 232 Computer Organization & Architecture
Homework 3 - Chapter 3 - 10 points
Due Date: 6/7/2023

| x | y | z | F |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |




$$f = x'y' + xy' + x'yz'$$



**METRO STATE
UNIVERSITY**

**ICS 232 Computer Organization & Architecture
Homework 3 - Chapter 3 - 10 points
Due Date: 6/7/2023**

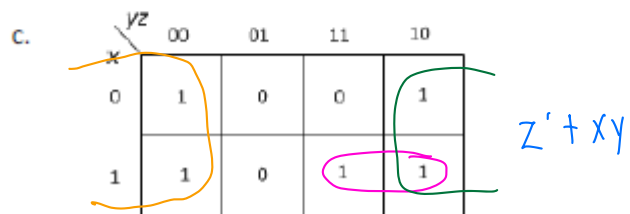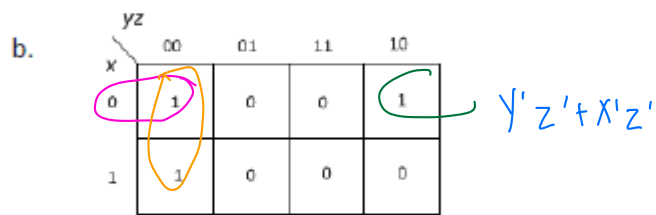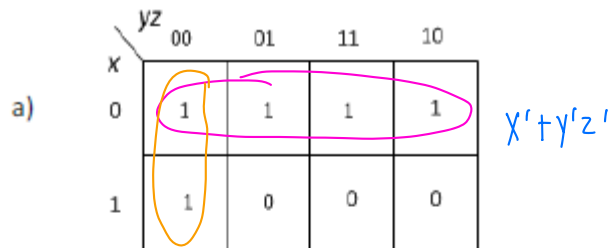29. Write a simplified expression for the Boolean function defined by each of the following Kmaps.






**METRO STATE
UNIVERSITY**

**ICS 232 Computer Organization & Architecture
Homework 3 - Chapter 3 - 10 points
Due Date: 6/7/2023**

46. Draw the combinational circuit that directly implements the following Boolean expression:

$$F(x,y,z) = x + xy + y'z$$

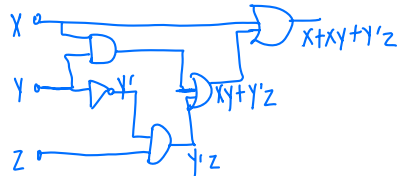

51. How many inputs does a decoder have if it has 64 outputs?

$$2^n = 64 \quad n = 6$$

52. How many control lines does a multiplexer have if it has 32 inputs?

$$5$$

Write a simple C program to sum the entries in an array and print out the sum and the average. The following may be used as a template:

```
#include <stdio.h>
#include <string.h>

int main(int argc, char ** argv)
{

    int average;
    int i;
    int size;
    int sum;

    static int numbers[] = {1, -1, 100, 32, 64, -96};

    for (i = 0; i < size; i++) {

    }

    printf("Sum = %d, Average = %d\n", sum, average);

    return (0);
```



METRO STATE
UNIVERSITY

ICS 232 Computer Organization & Architecture
Homework 3 - Chapter 3 - 10 points
Due Date: 6/7/2023

}

Prepare for next class by reading Chapter 4 – MARIE: An Introduction to a Simple Computer